

# PFC Totem-Pole Converter Control Strategy

Mohamed Gueni

August 31, 2024

## Contents

<b>1</b>	<b>Introduction</b>	<b>2</b>
<b>2</b>	<b>Control Strategy Overview</b>	<b>2</b>
2.1	Purpose . . . . .	2
2.2	Key Control Blocks . . . . .	2
<b>3</b>	<b>Voltage Regulation</b>	<b>2</b>
3.1	Purpose . . . . .	2
3.2	Implementation . . . . .	2
3.3	Controller . . . . .	3
3.4	Detailed Implementation . . . . .	3
<b>4</b>	<b>Power Factor Correction (PFC)</b>	<b>3</b>
4.1	Purpose . . . . .	3
4.2	Implementation . . . . .	4
4.3	Controller . . . . .	4
4.4	Detailed Implementation . . . . .	4
<b>5</b>	<b>Current Limiting</b>	<b>4</b>
5.1	Purpose . . . . .	4
5.2	Implementation . . . . .	5
5.3	Controller . . . . .	5
5.4	Detailed Implementation . . . . .	5
<b>6</b>	<b>Soft-Start</b>	<b>5</b>
6.1	Purpose . . . . .	5
6.2	Implementation . . . . .	6
6.3	Controller . . . . .	6
6.4	Detailed Implementation . . . . .	6
<b>7</b>	<b>Temperature Monitoring and Protection</b>	<b>6</b>
7.1	Purpose . . . . .	6
7.2	Implementation . . . . .	6

7.3	Controller . . . . .	7
7.4	Detailed Implementation . . . . .	7

## 1 Introduction

This document outlines the control strategy for a PFC Totem-Pole Converter with 3 legs, where each leg contains MOSFETs. The converter has an AC input and provides a 400V DC output. A coupled choke is placed on the line to improve the performance of the power factor correction.

## 2 Control Strategy Overview

### 2.1 Purpose

To regulate the output voltage, maintain high power factor, and ensure efficient operation of the PFC Totem-Pole Converter.

### 2.2 Key Control Blocks

The control strategy includes the following key blocks:

- Voltage Regulation
- Power Factor Correction (PFC)
- Current Limiting
- Soft-Start
- Temperature Monitoring

## 3 Voltage Regulation

### 3.1 Purpose

To maintain the desired DC output voltage of 400V despite variations in input voltage and load conditions.

### 3.2 Implementation

- **PI or PID Controller:** A Proportional-Integral (PI) or Proportional-Integral-Derivative (PID) controller processes the error between the actual output voltage and the reference voltage.
- **Feedback Loop:** Measures the output voltage and adjusts the duty cycle of the MOSFETs to maintain the output at 400V.

### 3.3 Controller

The output of the voltage regulation loop controls the duty cycle of the MOSFETs in the PFC circuit.

### 3.4 Detailed Implementation

- **Objective:** Ensure that the DC output voltage is regulated to 400V by adjusting the duty cycle of the MOSFETs.
- **Components Needed in PLECS:**
  - **PI or PID Controller:**
    - \* Processes the error between the measured output voltage and the reference voltage.
  - **Voltage Feedback:**
    - \* Measures the output voltage and provides feedback to the controller.
- **Block Diagram in PLECS:**
  - **Input:** Error signal from the output voltage regulation loop.
  - **Processing:** Use a PI or PID controller to process the error signal and adjust the MOSFET duty cycle.
  - **Output:** Control signals for the MOSFETs to maintain the desired output voltage.
- **Implementation Steps in PLECS:**
  1. **Create a PI or PID Controller block** that takes the voltage error signal as input.
  2. **Link the output of the Voltage Feedback** to the input of the PI or PID Controller.
  3. **Generate gate drive signals** for the MOSFETs based on the controller output.

## 4 Power Factor Correction (PFC)

### 4.1 Purpose

To correct the power factor by ensuring that the current drawn from the AC source is in phase with the input voltage, thus improving the efficiency of the converter.

## 4.2 Implementation

- **Current Feedback:** Measures the input current and provides feedback for phase and amplitude correction.
- **Control Algorithm:** Adjusts the duty cycle of the MOSFETs to correct the phase angle between the voltage and current.

## 4.3 Controller

A control algorithm such as a sliding mode controller or another advanced PFC technique can be used to ensure proper power factor correction.

## 4.4 Detailed Implementation

- **Objective:** Achieve a power factor close to unity by adjusting the duty cycle of the MOSFETs in response to current and voltage feedback.
- **Components Needed in PLECS:**
  - **Current Sensor:**
    - \* Measures the input current and provides feedback.
  - **Control Algorithm Block:**
    - \* Adjusts the duty cycle of the MOSFETs based on current and voltage feedback.
- **Block Diagram in PLECS:**
  - **Input:** Current feedback and voltage measurements.
  - **Processing:** Use the control algorithm to process the feedback and adjust the duty cycle.
  - **Output:** Control signals for the MOSFETs to correct the power factor.
- **Implementation Steps in PLECS:**
  1. **Create a Current Sensor block** to measure the input current.
  2. **Implement the Control Algorithm** to process current and voltage feedback.
  3. **Generate gate drive signals** for the MOSFETs based on the control algorithm output.

# 5 Current Limiting

## 5.1 Purpose

To protect the converter from excessive current that could damage components.

## 5.2 Implementation

- **Current Limiting Circuit:** Monitors the current and limits it to safe levels by adjusting the duty cycle of the MOSFETs or shutting down the converter.

## 5.3 Controller

Current protection logic integrated with the control loop or as a separate protection circuit.

## 5.4 Detailed Implementation

- **Objective:** Prevent damage by limiting the current to safe levels.
- **Components Needed in PLECS:**
  - **Current Sensor:**
    - \* Measures the current and provides feedback to the limiting circuit.
  - **Current Limiting Block:**
    - \* Adjusts the duty cycle or shuts down the converter based on current feedback.
- **Block Diagram in PLECS:**
  - **Input:** Current measurement feedback.
  - **Processing:** Use the current limiting block to process feedback and adjust the duty cycle or shut down.
  - **Output:** Adjusted control signals or shutdown command.
- **Implementation Steps in PLECS:**
  1. **Create a Current Sensor block** to measure the input current.
  2. **Implement the Current Limiting Block** to process the current feedback.
  3. **Generate control signals** based on the limiting block's output.

# 6 Soft-Start

## 6.1 Purpose

To gradually ramp up the output voltage and current to prevent inrush currents and ensure smooth startup.

## 6.2 Implementation

- **Soft-Start Circuit:** Gradually increases the duty cycle or switching frequency from a low value to the normal operating point during startup.

## 6.3 Controller

Typically integrated with the voltage regulation loop, where the reference voltage or duty cycle is gradually ramped up.

## 6.4 Detailed Implementation

- **Objective:** Smoothly ramp up the operation of the converter to avoid inrush currents.
- **Components Needed in PLECS:**
  - **Soft-Start Block:**
    - \* Gradually increases the duty cycle or frequency during startup.
- **Block Diagram in PLECS:**
  - **Input:** Soft-start control signal.
  - **Processing:** Ramp up the duty cycle or frequency.
  - **Output:** Gradually increased control signals for the MOSFETs.
- **Implementation Steps in PLECS:**
  1. **Create a Soft-Start Block** that controls the ramp-up of the duty cycle or frequency.
  2. **Link the Soft-Start Block** to the control signals for the MOSFETs.

# 7 Temperature Monitoring and Protection

## 7.1 Purpose

To protect the MOSFETs and other critical components from overheating.

## 7.2 Implementation

- **Thermal Sensors:** Measure the temperature of the MOSFETs and other critical components.
- **Thermal Protection Logic:** Reduces the duty cycle, shuts down the converter, or engages cooling mechanisms if temperatures exceed safe limits.

### 7.3 Controller

Thermal protection circuit integrated with the main control loop or as a separate module.

### 7.4 Detailed Implementation

- **Objective:** Ensure safe operation by monitoring and managing temperatures.
- **Components Needed in PLECS:**
  - **Temperature Sensors:**
    - \* Measure temperatures and provide feedback.
  - **Thermal Protection Block:**
    - \* Adjusts the operation based on temperature feedback.
- **Block Diagram in PLECS:**
  - **Input:** Temperature feedback.
  - **Processing:** Use thermal protection logic to adjust operation or shut down.
  - **Output:** Adjusted control signals or shutdown command.
- **Implementation Steps in PLECS:**
  1. **Create Temperature Sensors** to monitor critical components.
  2. **Implement Thermal Protection Logic** based on sensor feedback.
  3. **Generate control signals** or shutdown commands based on the protection logic.